# 开关电源EMI技术交流

En Li

Mar. 2022




### 主要内容

- ▶ 电磁干扰(EMI)分析及处理方案
  - Reducing The Noise Source
  - Improving the Noise Path
- ➤ MPS产品介绍




### EMI 危害

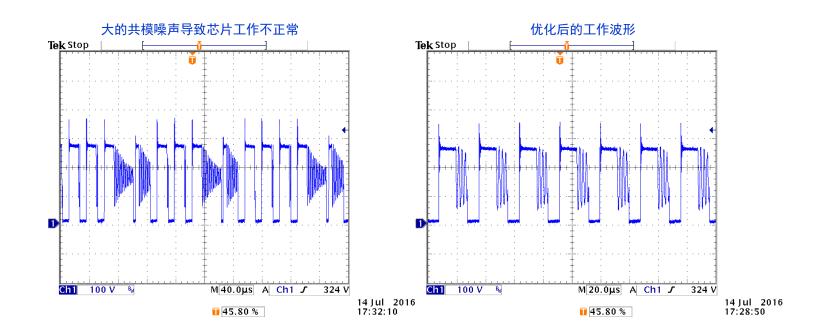





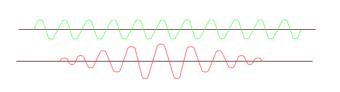





Noise Source Coupling Path Receptor





**Suppress** noise source




Cut off coupling path




Make receptor insensitive




### 开关电源中的主要噪声源

 

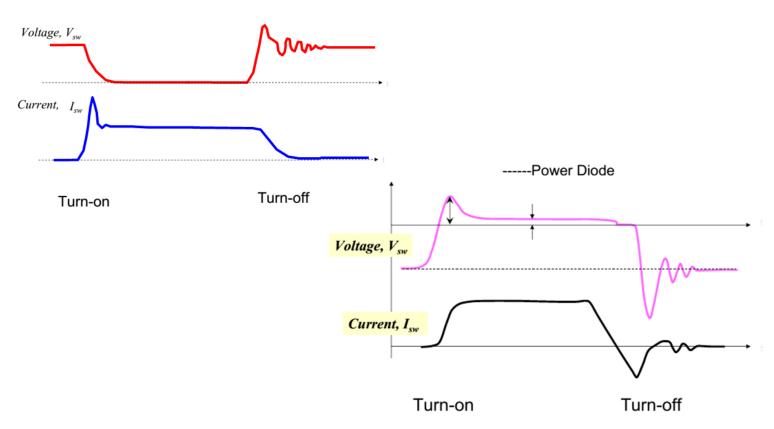



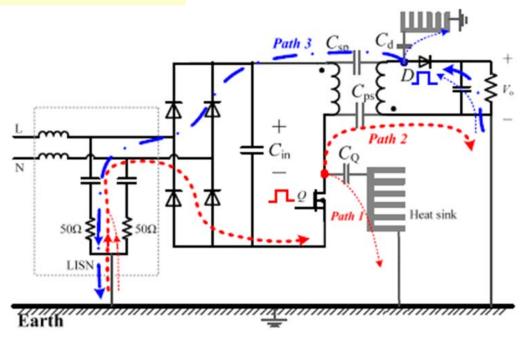The main noise sources and coupling paths in flyback converter




Noise Source: MOSFET, Diode

Coupling path: parasitic capacitance, PCB routing


Load:  $25\Omega$  resistor



#### 差模噪声耦合路径

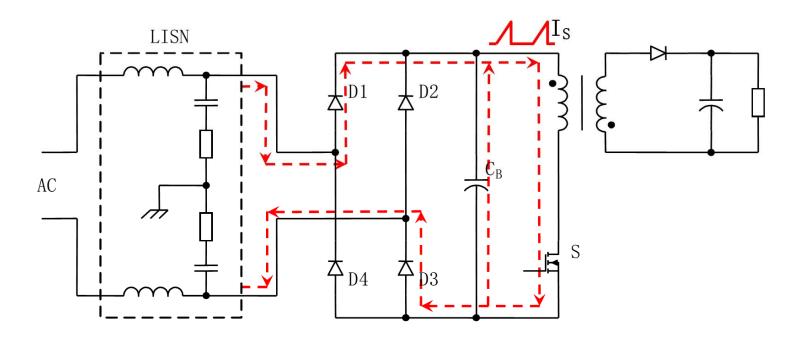



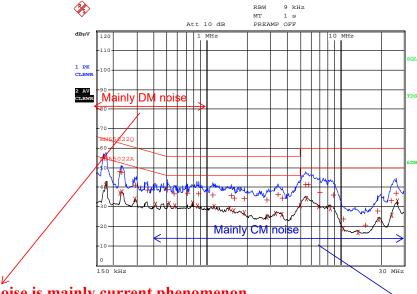

Differential mode noise is mainly current phenomenon and is driven by rapidly changing current signals.

- >DM = f (di/dt)
- ➤DM is associated with voltage across bulk cap created due to switching currents


Common mode noise is mainly voltage phenomenon and is driven by rapidly changing voltage signals

- ightharpoonup CM = f(dV/dt)
- > CM can be associated with capacitive coupling and displacement currents external to the power supply




#### 传导电磁干扰改善步骤

❖ 用滤波器来区分共模与差模干扰;

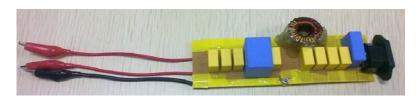

❖ 根据频率分布来确定主导的电磁干扰;

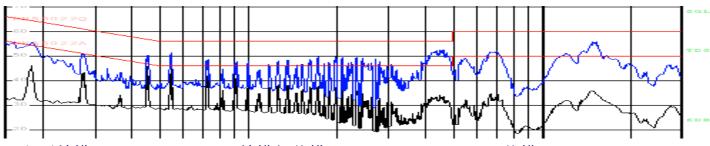


- 主要差模
- 低次谐波
- 交流整流相关
- 近场干扰
- ...

- 差模与共模
- 高次谐波
- 低频震荡
- 近场干扰
- ...

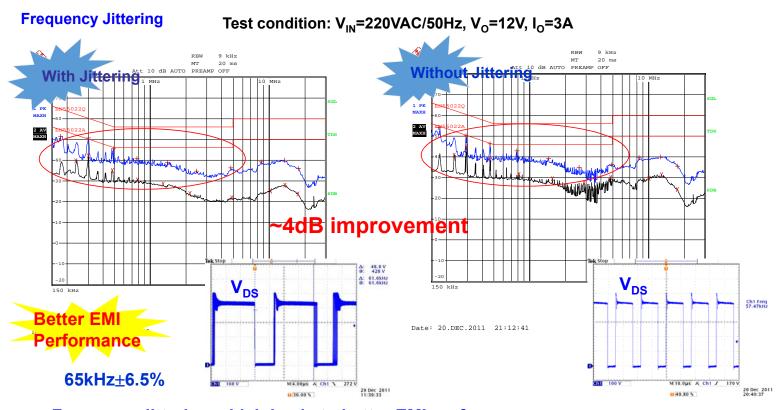
- 共模
- 近场干扰
- 高频振荡
- 开关上升下降沿
- •二极管反向恢复
- Layout
- ...





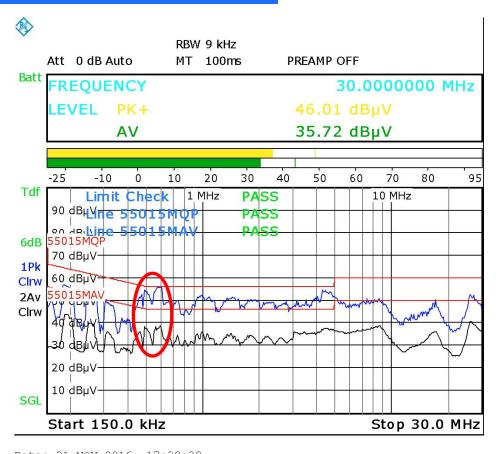Frequency jittering which leads to better EMI performance.






Date: 21.NOV.2016 17:38:38



Test Condition: Vin=230VAC, Output=20V/2.25A

L=365uH, N=7, K@90VAC= $I_{ripple}/I_{peak}$ =1.

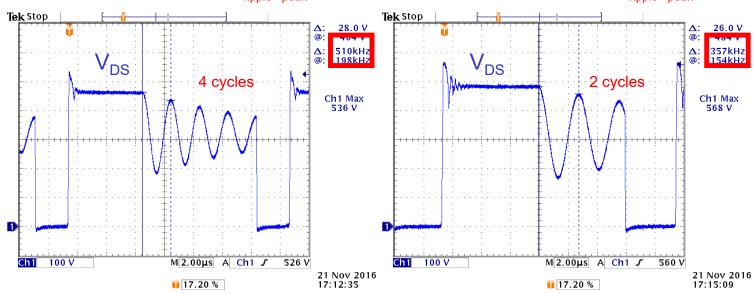L=740uH, N=8, K@90VAC= $I_{ripple}/I_{peak}$ =0.7.




When the system enter DCM, the oscillation is determined by primary inductance L and parasitic capacitor (MOS and transformer ).

The oscillation frequency is hundreds kHz, it's hard to get enough EMI margin.




Test Condition: Vin=230VAC, Output=20V/2.25A

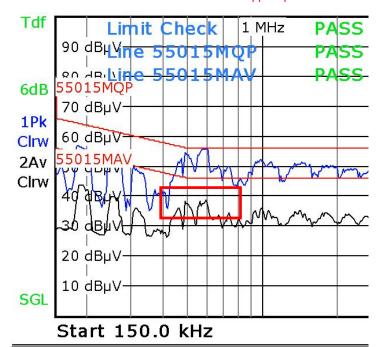L=365uH, N=7, K@90VAC= $I_{ripple}/I_{peak}$ =1.



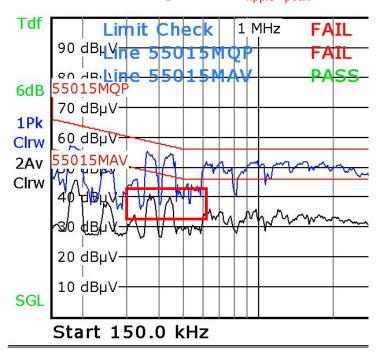
L=740uH, N=8, K@90VAC=I<sub>ripple</sub>/I<sub>peak</sub>=0.7.




Increasing inductor can reduce frequency, and chooses smaller K can reduce the cycles.



❖ 改善效果快速判定方法

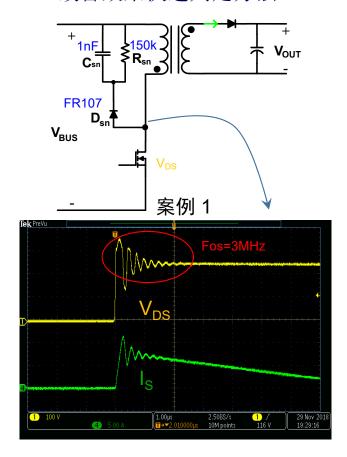


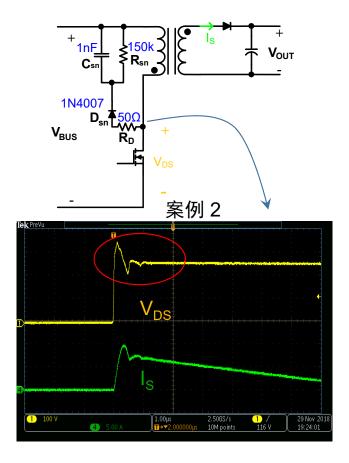



通过改变原边Mosfet关断时VDS的震荡来改善EMI


❖ 改善效果快速判定方法

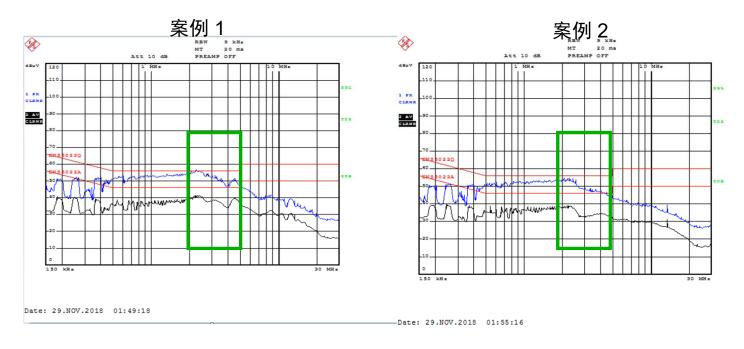

传导EMI在3MHz段有~5dB改善




❖ 改善效果快速判定方法

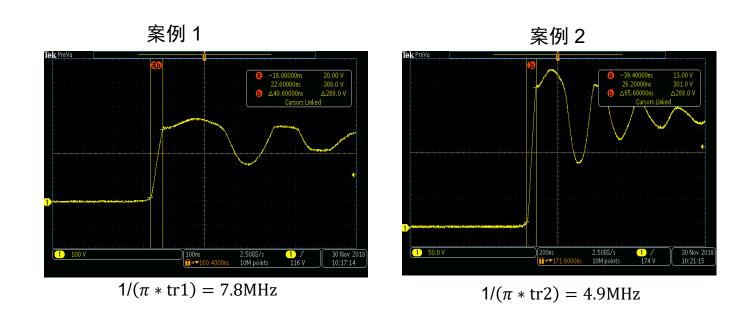

改变VDS的上升/下降斜率来改善EMI




❖ 改善效果快速判定方法

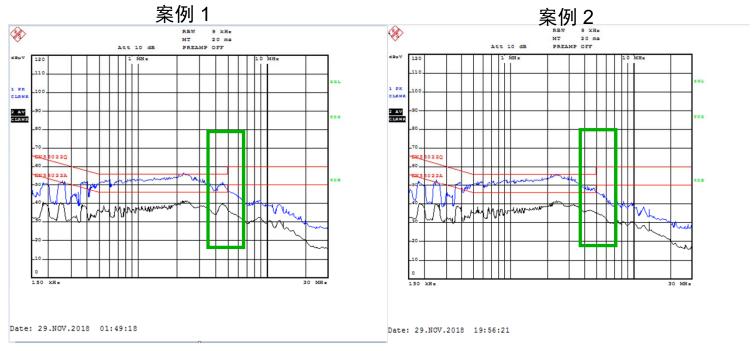


传导EMI在5MHz段有~3dB改善



❖ 减小传导电磁干扰途径一 - 改善电路板的布线

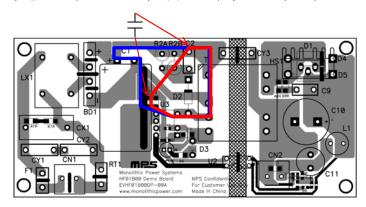

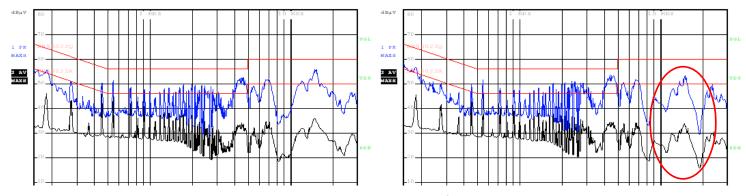


传导EMI在10MHz+段有~3dB改善




- Y capacitors
- Common mode filters (Common Choke)
- Better transformer construction techniques aimed at reducing CM noise at its source thus reducing the need for heavy filtering using CM line filters and Y capacitors
  - Basic transformer construction recommendations
  - Use of Shield windings
- Near field coupling



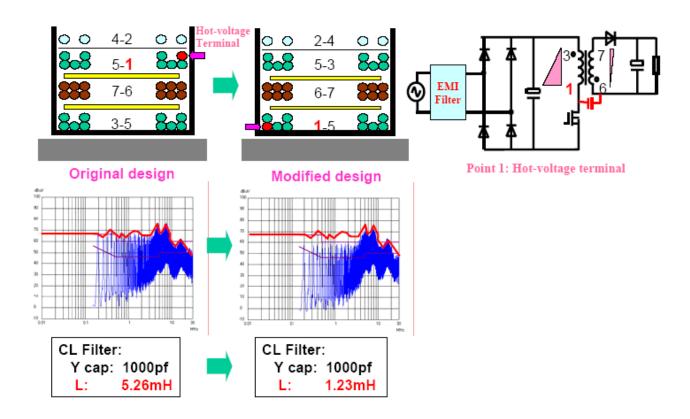Effects of terminal position on conducted EMI noise






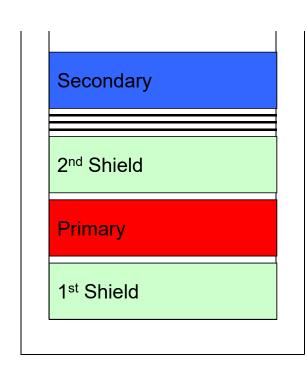

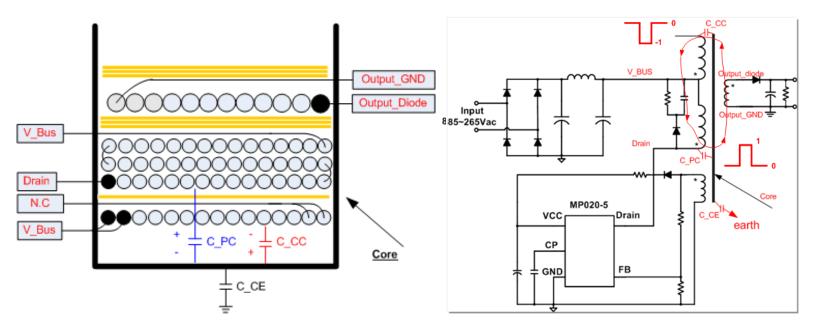
- Generally 2 separate shield windings are recommended
- 1st shield is the "Cancellation Shield winding" and is normally placed between core and primary winding
- 2<sup>nd</sup> shield is the "Balanced Shield winding" placed between the Primary and the Secondary windings





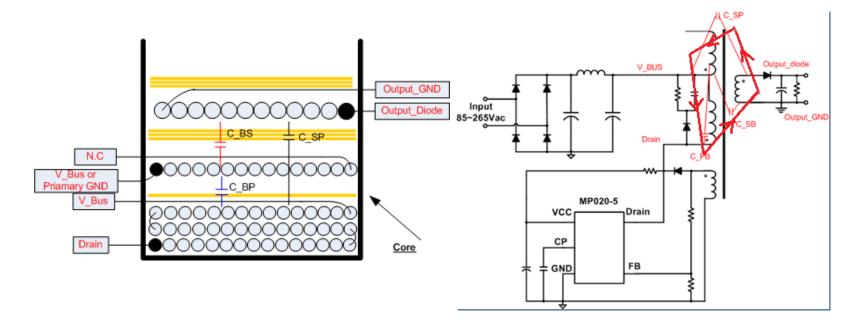- Cancels out the P-E noise mechanism
- Generally uses around ½ the number of turns in the first layer of primary winding (should be tuned by the evaluation)
- Both the primary and cancellation windings induce displacement currents in opposite directions, leading to "cancellation" of displacement currents within the LISN







- Used to reduce P-S coupling mechanism
- Generally uses 1-2 turns less than the secondary winding
- Principle is to "balance" the potential at the primary & secondary side thereby reducing noise coupling



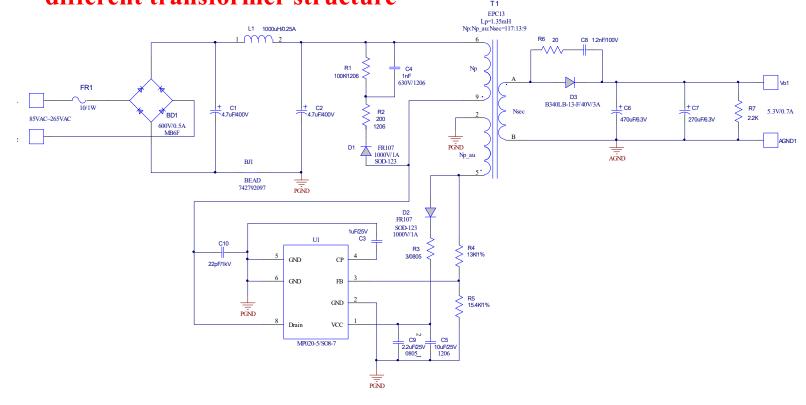
The following test results is based on the same SCH except the different transformer structure





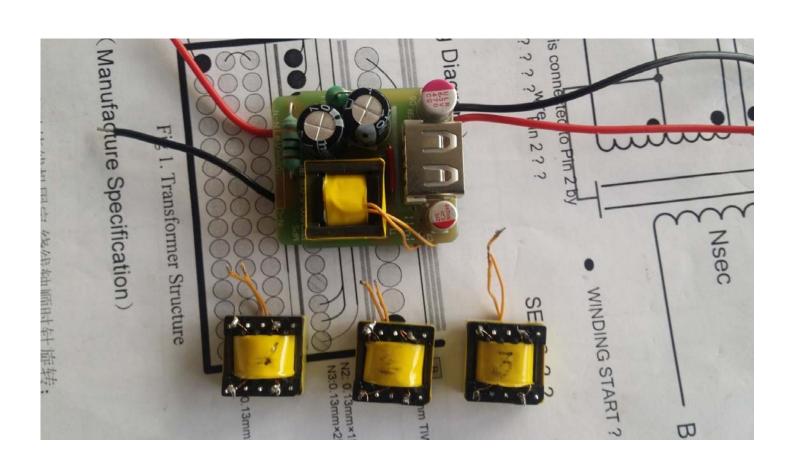




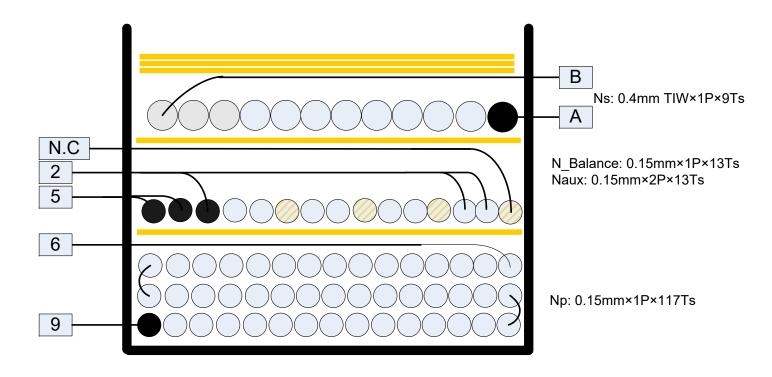

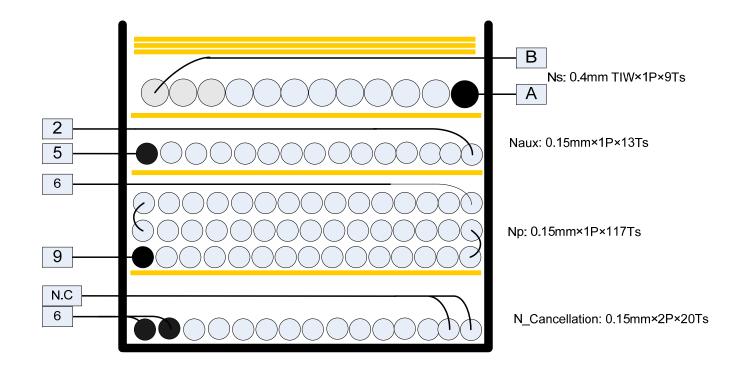
Xformer #1 W/I balance winding, which wound with the auxiliary winding






**Xformer #2 W/I cancellation winding** 




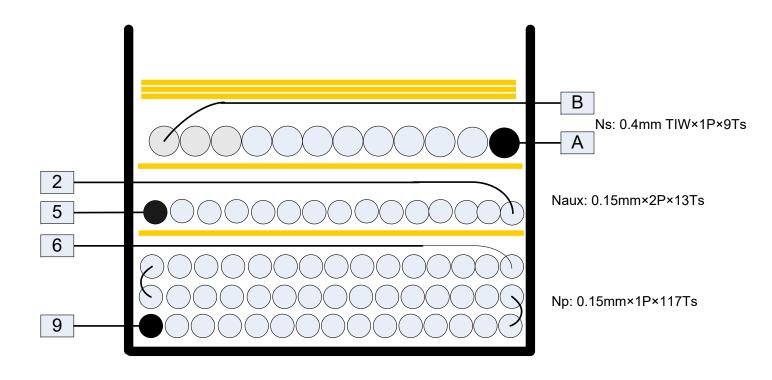

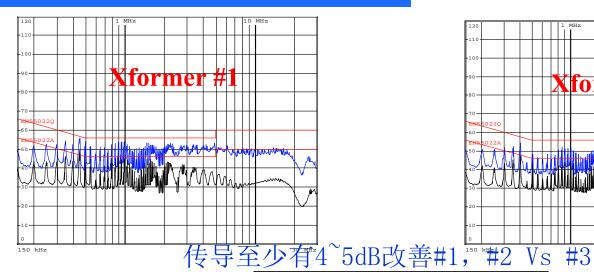
Xformer #3 W/O any cancellation or balance winding






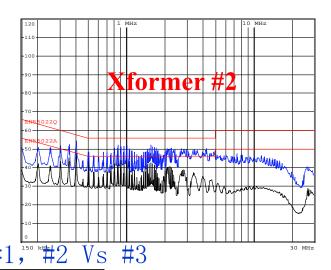


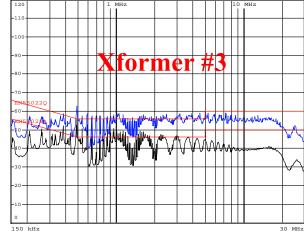Test conditions:
220Vac input
5.3V/0.7A output
L line






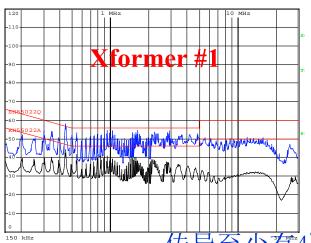

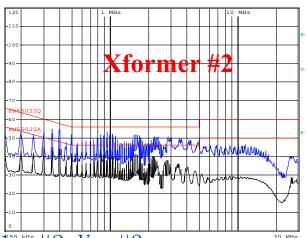


传导至少有<sup>4</sup><sup>2</sup>5dB改善#1<sup>5</sup>0, kHz #2 Vs #3

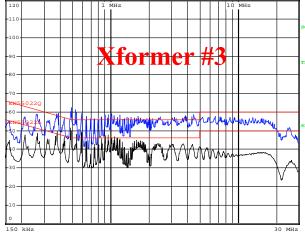Test conditions:
220Vac input
5.3V/0.7A output
N line






❖ 减小传导电磁干扰途径 – 改变变压器结构

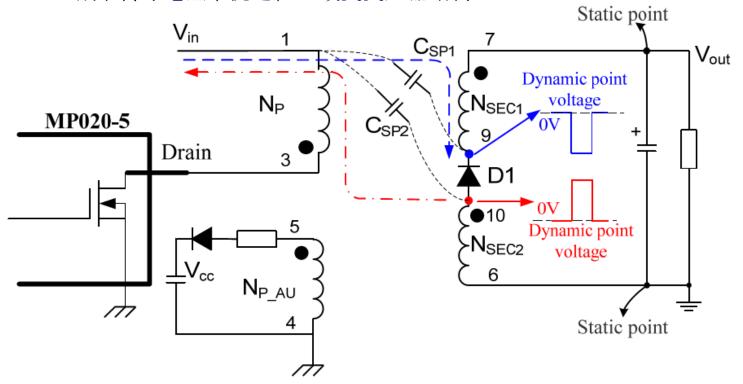




❖ 减小传导电磁干扰途径四 - 改变变压器结构

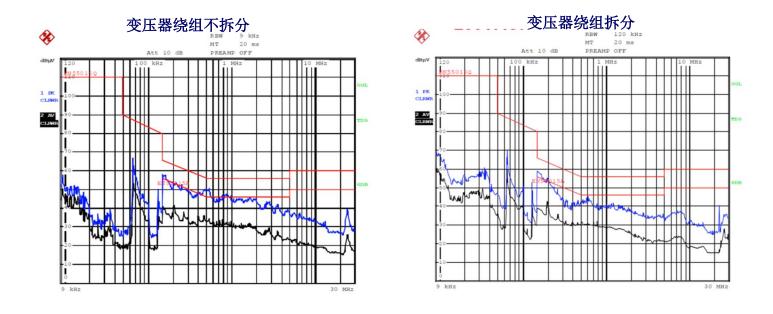

在通过将变压器的一个绕组拆分为两部分,200kHz 至 5MHz 有大约 6dB 的改善.




❖ 近场耦合效应

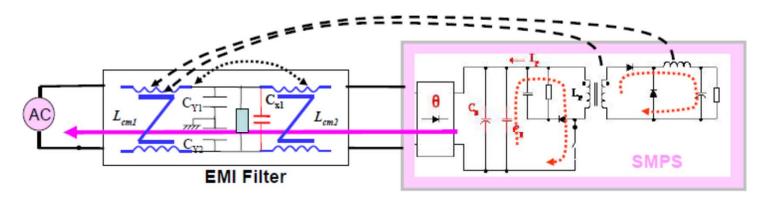



- ☐ Coupling inside EMI filter: CMC to CMC, CMC to Cap, Cap to Cap.
- □ Coupling between EMI filter and transformer/inductor.



#### ❖ 近场耦合效应

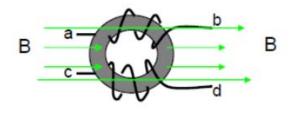

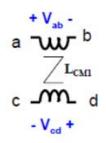

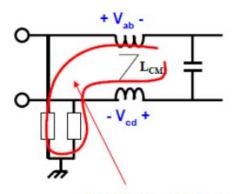



Produce DM noise




❖ 近场耦合效应

方案1 改变共模电感方向 方案2 共模电感双线并绕 方案3 共模电感前加电容

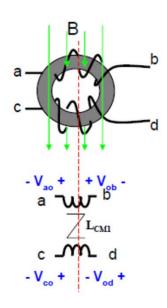

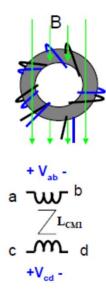

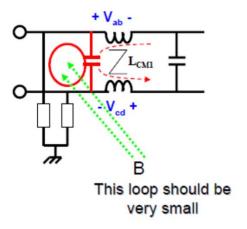




❖ 近场耦合效应








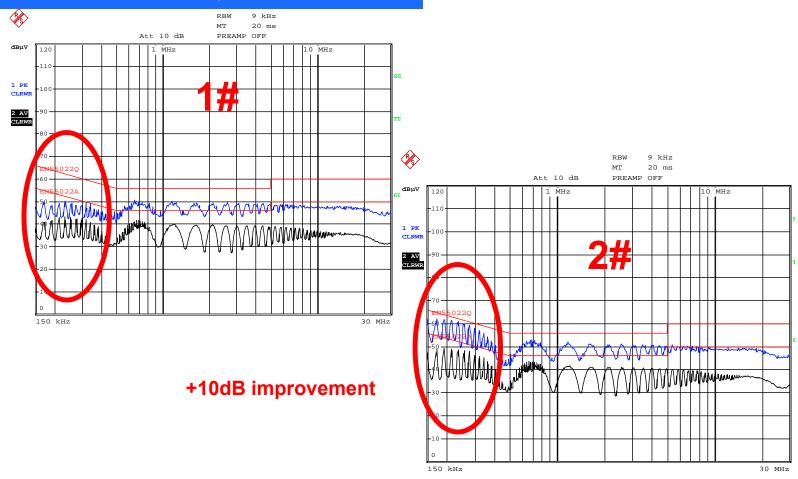



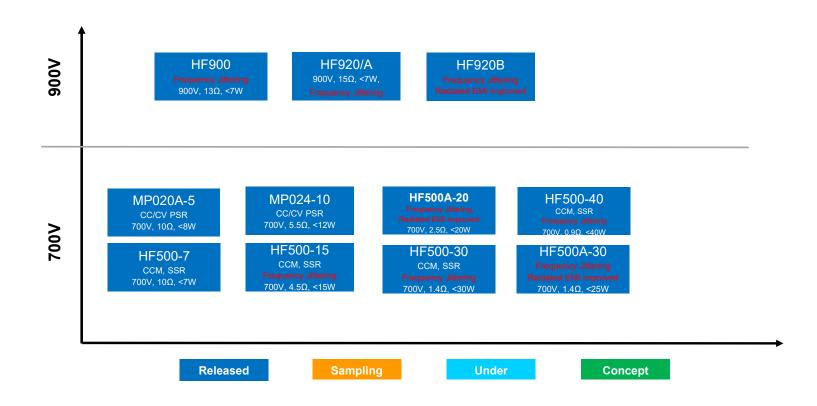
### AC/DC Flyback regulator with integrated MOSFET, up to 40W




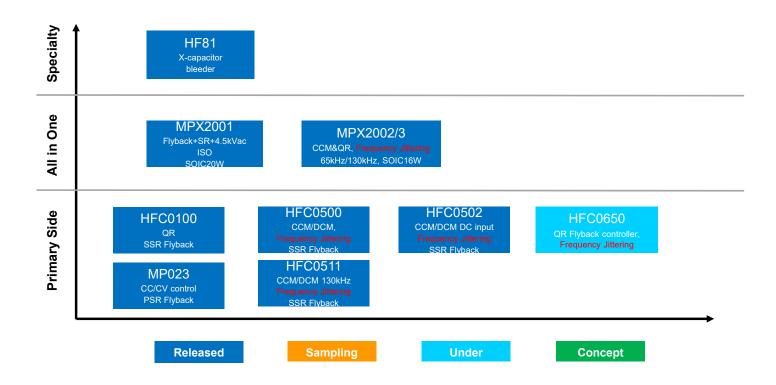
#### AC/DC Flyback Controller, up to 140W





# Q&A

